

Assignment on DLD for 48th Batch

1. A combinational circuit is defined by the following three Boolean functions

$$F1 = x'y'z' + xz \quad F2 = xy'z' + x'y \quad F3 = x'y'z + xy.$$

Design the circuit with a decoder and external gates.

2. Obtain the primitive flow table for an asynchronous circuit that has 2 input's x, y and output z. an output $z=1$, is to occur only during the input state $xy=01$ and then if and only if the input state $xy=01$ is preceded by the input sequence $xy=01, 00, 10, 00, 10, 00$.

3. A sequential circuit has 2D ff's A and B an input x and output y is specified by the following next state and output equations.

a. $A(t+1) = Ax + Bx$

b. $B(t+1) = A'x$

c. $Y = (A+B)x'$

- (i) Draw the logic diagram of the circuit.
- (ii) Derive the state table.
- (iii) Derive the state diagram.