



***INSTITUTE OF INFORMATION TECHNOLOGY***  
***JAHANGIRNAGAR UNIVERSITY***

**Number of Assignment : 01**

**Name of Assignment : Designing Combinational Logic Circuits.**

**Course Title : Digital Logic Design**

**Course Code : ICT – 2103**

**Submission Date : 25/08/2020**

**Submitted To**

Dr. Md. Sazzadur Rahman

Assistant Professor

IIT – JU

**Submitted By**

MD. Shakil Hossain

Roll – 2023

2<sup>nd</sup> year 1<sup>st</sup> Semester

IIT - JU

Problem 1: Due to the low number of People in the mosque of our village, Congregation is not held many times. Design a logic circuit is when the congregation will be and when it will not be. Four inputs A, B, C and D whose output will be High only when a majority of the inputs are High.

Solution:

Step 1. Truth table

on the basis of the Problem statement the output x should be 1 when ever three or more inputs are 1 for all other cases the output should be 0.

A	B	C	D	x	A	B	C	D	x
0	0	0	0		1	0	0	0	
0	0	0	1		1	0	0	1	
0	0	1	0		1	0	1	0	
0	0	1	1		1	0	1	1	$1 \rightarrow \bar{A}\bar{B}CD$
0	1	0	0		1	1	0	0	
0	1	0	1		1	1	0	1	$1 \rightarrow AB\bar{C}D$
0	1	1	0		1	1	1	0	$1 \rightarrow ABC\bar{D}$
0	1	1	1	$1 \rightarrow \bar{A}BCD$	1	1	1	1	$1 \rightarrow ABCD$

Step 2. Write the AND term for each case where the output is a 1.

$$\bar{A}BCD, A\bar{B}CD, AB\bar{C}D, ABC\bar{D}, ABCD$$

Step 3. Write the sum-of-Products expression for the output.

$$x = \bar{A}BCD + A\bar{B}CD + AB\bar{C}D + ABC\bar{D} + ABCD$$

Step 4. Simplify the output expression.

$$x = \bar{A}BCD + A\bar{B}CD + AB\bar{C}D + ABC\bar{D} + ABCD$$

$$= \bar{A}BCD + AB\bar{C}D + A\bar{B}CD + ABCD + AB\bar{C}D + ABCD + ABC\bar{D} + ABCD$$


$$= BCD(\bar{A} + A) + ACD(\bar{B} + B) + ABD(\bar{C} + C) + ABC(\bar{D} + D)$$

Each term in Parentheses is equal to 1, so we have

$$x = BCD + ACD + ABD + ABC$$



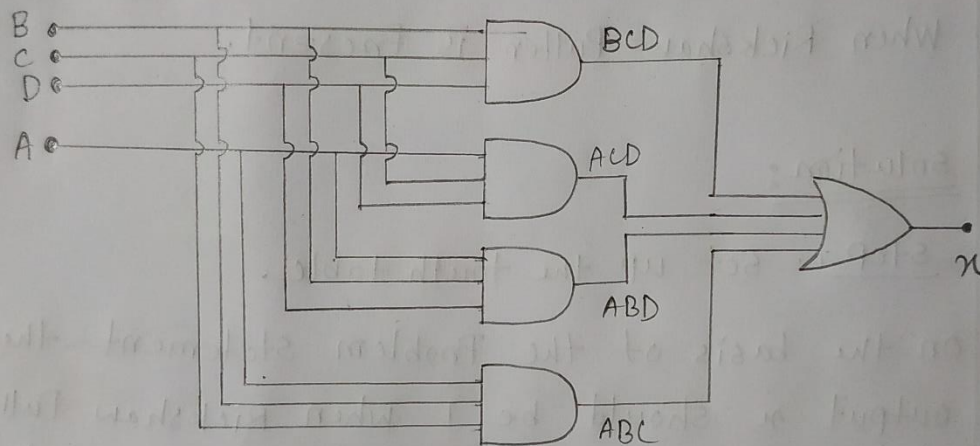Step 5. Implement the circuit for the final expression.



$$X = BCD + ACD + ABD + ABC$$

Problem 2. When a rickshaw will run and when it will not run. Design a logic circuit that has three inputs, Rickshaw Puller, Passengers 1, Passenger 2. and whose output will be High ~~on~~ when Rickshaw Puller is Present.

Solution:

Step 1. Set up the truth table.

On the basis of the Problem Statement the output  $x$  should be 1 when Rickshaw Puller inputs are 1. for all other cases the output should be 0.

let  $A = \text{Rickshaw Puller}$

$B = \text{Passenger 1}$

$C = \text{Passenger 2}$

A	B	C	x
0	0	0	
0	0	1	
0	1	0	
0	1	1	
1	0	0	$1 \rightarrow A\bar{B}\bar{C}$
1	0	1	$1 \rightarrow A\bar{B}C$
1	1	0	$1 \rightarrow AB\bar{C}$
1	1	1	$1 \rightarrow ABC$

Step 2. Write the AND term for each case where the output is a 1.

$$A\bar{B}\bar{C}, A\bar{B}C, AB\bar{C}, ABC$$

Step 3. Write the Sum-of-Products expressions

$$x = A\bar{B}\bar{C} + A\bar{B}C + AB\bar{C} + ABC$$



Step 4. simplify expression.

$$\begin{aligned}x &= A\bar{B}\bar{C} + A\bar{B}C + AB\bar{C} + ABC \\&= A\bar{B}\bar{C} + AB\bar{C} + A\bar{B}C + ABC \\&= A\bar{C}(\bar{B}+B) + AC(\bar{B}+B) \\&= A\bar{C} + AC \\&= A(\bar{C}+C) \\&= A\end{aligned}$$

Step 5. Implement the circuit for the final expression.

No Circuit is required.

Problem 3. Shakil, Nahid and Tokee are three friends. They will go to Sylhet. If more of ~~more~~ of them go they will go.

Solution:

Step 1. set up the truth table

let  $A = \text{Shakil}$

$B = \text{Nahid}$

$C = \text{Tokee}$

On the basis of the Problem statement the output  $x$  should be 1 when-ever two or more inputs are 1 for all other cases the output should be 0.



A	B	C	x
0	0	0	
0	0	1	
0	1	0	
0	1	1	1 $\rightarrow \bar{A}BC$
1	0	0	
1	0	1	1 $\rightarrow A\bar{B}C$
1	1	0	1 $\rightarrow AB\bar{C}$
1	1	1	1 $\rightarrow ABC$

Step 2. Write the AND term for each case where the output is a 1.

$$\bar{A}BC, A\bar{B}C, AB\bar{C}, ABC$$

Step 3: Write the Sum-of-Products expression for the output.

$$x = \bar{A}BC + A\bar{B}C + AB\bar{C} + ABC$$

step 4. simplify the output expression.


$$x = \bar{A}BC + A\bar{B}C + AB\bar{C} + ABC$$

$$= \bar{A}BC + ABC + A\bar{B}C + ABC + AB\bar{C} + ABC$$

$$= BC(\bar{A} + A) + AC(\bar{B} + B) + AB(\bar{C} + C)$$

$$= BC + AC + AB$$

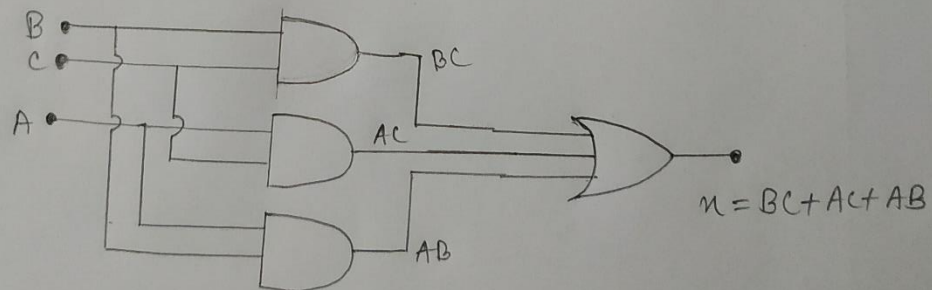step 5. Implement the circuit for the final expression.



Problem 4: IIT 10 batch female class Representative will be elected. Maysha, Monisha, Sanjida and Tasnia are 4 candidates. The output will be High when Maysha is High. The output will be High when a majority of the inputs are High. Design the logic circuit to Produce a High at output signal  $n$  for the stated conditions.

Solution:

Step 1. Set up the truth table

let  $A = \text{Maysha}$

$B = \text{Monisha}$

$C = \text{Sanjida}$

$D = \text{Tasnia}$

On the basis of the Problem statement the output  $n$  should be 1 when  $A$  is 1 and three or more inputs are 1 for all other cases the output should be 0.



A	B	C	D	$x$
0	0	0	0	
0	0	0	1	
0	0	1	0	
0	0	1	1	
0	1	0	0	
0	1	0	1	
0	1	1	0	
0	1	1	1	1 $\rightarrow \bar{A}BcD$
1	0	0	0	1 $\rightarrow A\bar{B}\bar{C}\bar{D}$
1	0	0	1	1 $\rightarrow A\bar{B}\bar{C}D$
1	0	1	0	1 $\rightarrow A\bar{B}C\bar{D}$
1	0	1	1	1 $\rightarrow A\bar{B}CD$
1	1	0	0	1 $\rightarrow AB\bar{C}\bar{D}$
1	1	0	1	1 $\rightarrow AB\bar{C}D$
1	1	1	0	1 $\rightarrow ABC\bar{D}$
1	1	1	1	1 $\rightarrow ABCD$

Step 2. Write the AND term for each case where output is a 1.

$\bar{A}BcD, A\bar{B}\bar{C}\bar{D}, A\bar{B}\bar{C}D, A\bar{B}C\bar{D}, A\bar{B}CD, AB\bar{C}\bar{D},$   
 $AB\bar{C}D, ABC\bar{D}, ABCD$


Step 3. Write the sum-of-Products expression for the output.

$$x = \bar{A}BCD + A\bar{B}\bar{C}\bar{D} + A\bar{B}\bar{C}D + A\bar{B}C\bar{D} + A\bar{B}CD + AB\bar{C}\bar{D} + AB\bar{C}D + ABC\bar{D} + ABCD$$

Step 4. Simplify the output

$$\begin{aligned} x &= \bar{A}BCD + A\bar{B}\bar{C}(\bar{D}+D) + A\bar{B}C(\bar{D}+D) + AB\bar{C}(\bar{D}+D) + ABC(\bar{D}+D) + ABCD \\ &= \bar{A}BCD + A\bar{B}\bar{C} + A\bar{B}C + AB\bar{C} + ABC + ABCD \\ &= \bar{A}BCD + A\bar{B}(\bar{C}+C) + AB(\bar{C}+C) + ABCD \\ &= \bar{A}BCD + A\bar{B} + AB + ABCD \\ &= \bar{A}BCD + A(\bar{B}+B) + ABCD \\ &= \bar{A}BCD + ABCD + A \\ &= BCD(\bar{A}+A) + A \\ &= BCD + A \end{aligned}$$

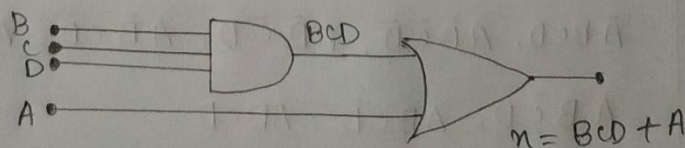Step 5. Implement the circuit for the final expression.



---

THE END